


Started on	Thursday, 18 January 2024, 2:00 PM
State	Finished
Completed on	Thursday, 18 January 2024, 2:10 PM
Time taken	9 mins 54 secs
Marks	2.00/4.00
Grade	5.00 out of 10.00 (50%)

Question 1

Incorrect

Mark 0.00 out of 1.00

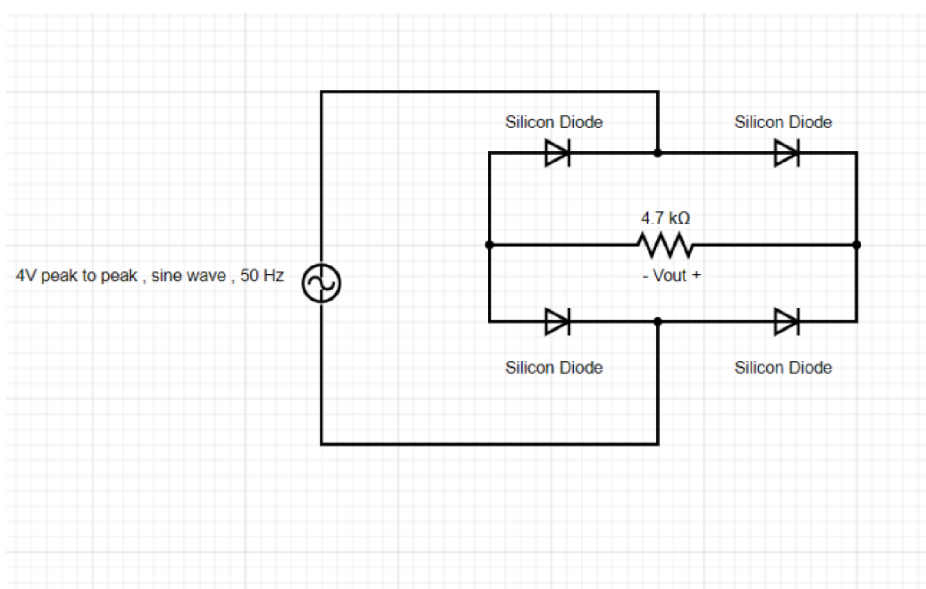1. Given is a circuit of bridge rectifier made using 4 Silicon diodes. The Silicon diodes have a cut-in voltage of 0.7 V but are **ideal** otherwise. The peak value of voltage drop appearing across the 4.7 K Ω resistor in Volts (V) is equal to .



Answer: 1.2

The correct answer is: 0.6

Question 2

Correct

Mark 1.00 out of 1.00

2. An Oscillator circuit has been designed using an **Ideal** Op-Amp and **Ideal** diodes as shown in the figure. The Upper Trip Point and Lower Trip Point for the circuit in Volts (V) **respectively** are .

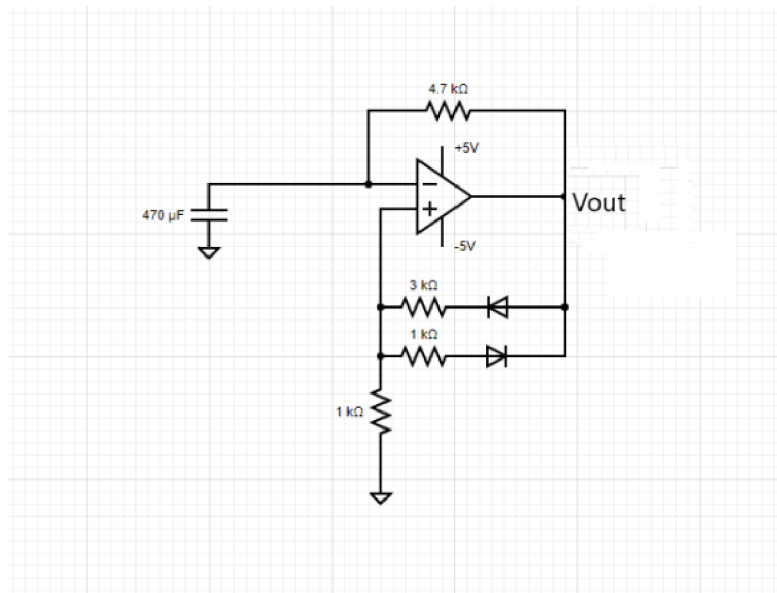


Figure 2: Oscillator circuit

- ☐ a. 1.25 and -1.25
- ☐ b. -2.5 and 1.25
- ☒ c. 1.25 and -2.5
- ☐ d. 2.5 and -2.5

Your answer is correct.

The correct answer is: 1.25 and -2.5

Question 3

Incorrect

Mark 0.00 out of 1.00

3. The figure shows a circuit designed using an Ideal Op-Amp. The Silicon diode used in the circuit has a cut-in voltage of 0.7 V but is otherwise **ideal**. The peak value of the voltage appearing across the $4.7\text{K } \Omega$ resistor in Volts (V) is equal to .

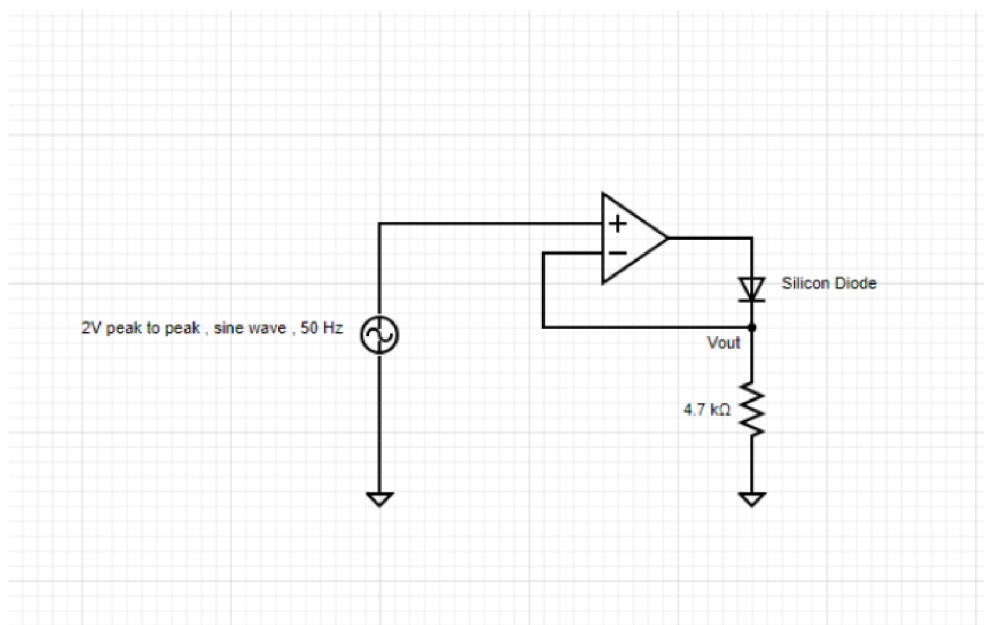


Figure 3: A very nice circuit

Answer: 2


The correct answer is: 1

Question 4

Correct

Mark 1.00 out of 1.00

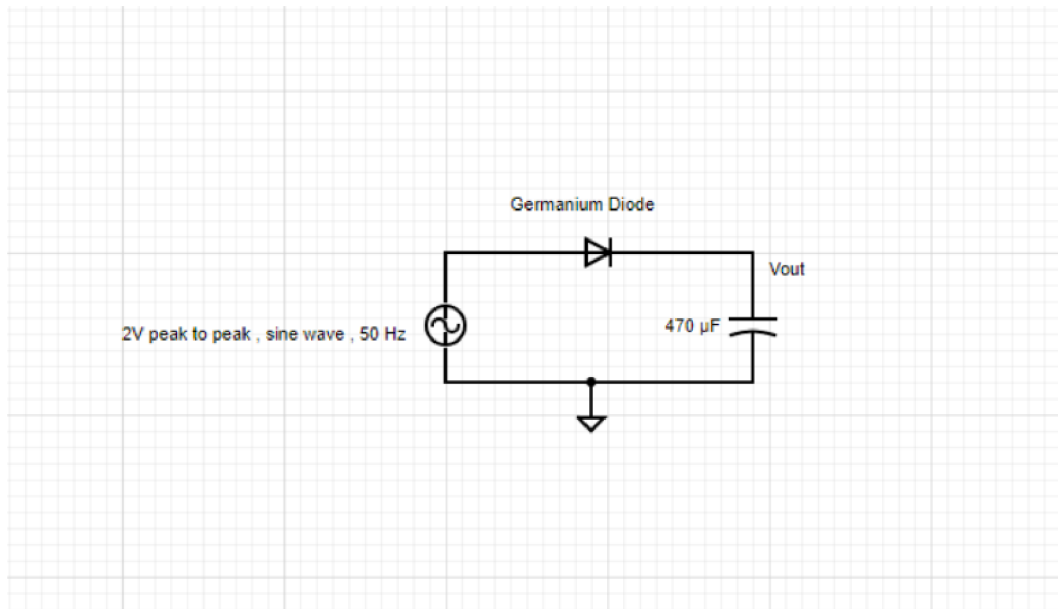4. The figure shows a circuit designed using an Ideal Op-Amp, a Germanium Diode and a $470\text{ }\mu\text{F}$ capacitor. The Germanium diode used in the circuit has a cut-in voltage of 0.3 V but is otherwise **ideal**. The V_{out} in **steady state** is .



- ☐ a. A **D.C.** signal with some negative amplitude
- ☐ b. Positive Half Cycle of Sine Wave only.
- ☐ c. Negative Half Cycle of Sine Wave only.
- ☒ d. A **D.C.** signal with some positive amplitude.

Your answer is correct.

The correct answer is: A **D.C.** signal with some positive amplitude.

Jump to...

[< Previous Activity](#)

[Next Activity >](#)

